




Computer Organisation and Architecture


Smruti Ranjan Sarangi,
IIT Delhi

Chapter 8 Processor Design

Also available as  Book

Computer Organisation and Architecture


Smruti Ranjan Sarangi

 

These slides are meant to be used along with the book: Computer Organisation and Architecture, Smruti Ranjan Sarangi, McGrawHill 2015
Visit: <http://www.cse.iitd.ernet.in/~srsarangi/archbooksoft.html>

Outline

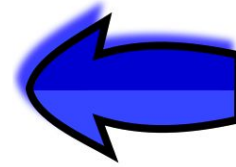
- * Overview of a Processor
- * Detailed Design of each Stage
- * The Control Unit
- * Microprogrammed Processor
- * Microassembly Language
- * The Microcontrol Unit



Processor Design


- * The aim of **processor design**
 - * **Implement** the entire SimpleRisc ISA
 - * **Process** the binary format of instructions
 - * Provide as much of **performance** as possible
- * Basic Approach
 - * Divide the processing into **stages**
 - * Design each **stage** separately

A Car Assembly Line

 

- * Similar to a car **assembly line**
 - * Cast raw **metal** into the **chassis** of a car
 - * Build the **Engine**
 - * Assemble the **engine** and the **chassis**
 - * Place the **dashboard**, and **upholstery**

A Processor Divided Into Stages

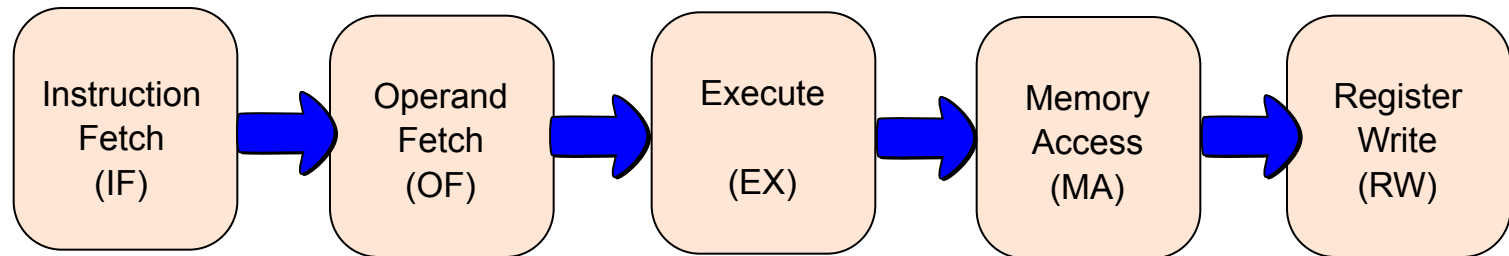

* Instruction **Fetch** (IF)

- * **Fetch** an instruction from the instruction memory
- * **Compute** the address of the next instruction

Operand Fetch (OF) Stage

* Operand Fetch (OF)

- * **Decode** the instruction (break it into fields)
- * **Fetch** the register operands from the register file
- * **Compute** the **branch target** (PC + offset)
- * **Compute** the **immediate** (16 bits + 2 modifiers)
- * Generate **control signals** (we will see later)

Execute (EX) Stage

* The EX Stage


- * Contains an **Arithmetic-Logical Unit (ALU)**
 - * This unit can perform all **arithmetic** operations (add, sub, mul, div, cmp, mod), and **logical** operations (and, or, not)
- * Contains the **branch** unit for computing the branch condition (beq, bgt)
- * Contains the **flags** register (updated by the cmp instruction)

MA and RW Stages

- * MA (Memory Access) Stage
 - * Interfaces with the memory system
 - * Executes a load or a store
- * RW (Register Write) Stage
 - * Writes to the register file
 - * In the case of a call instruction, it writes the return address to register, ra

Outline

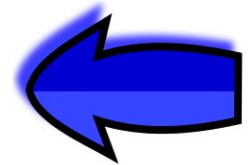- * Outline of a Processor
- * Detailed Design of each Stage
- * The Control Unit
- * Microprogrammed Processor
- * Microassembly Language
- * The Microcontrol Unit



Design Goals

**Functional Completeness and
Correctness**


Performance

Power

Area

Simplicity
Ease of Analysis and Debugging

Instruction Fetch (IF) Stage

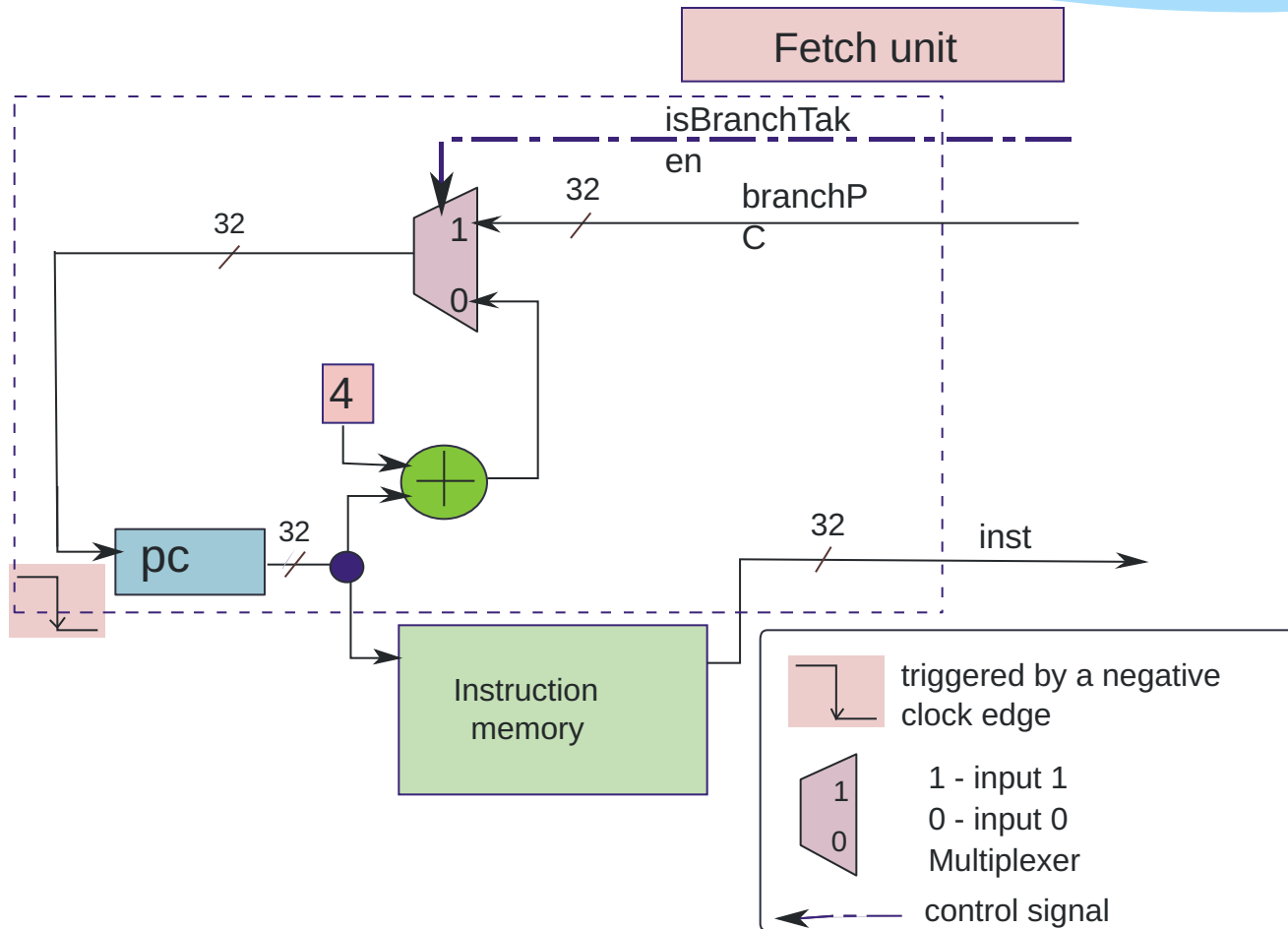

The Fetch unit

- * The **pc** register contains the **program counter** (**negative edge** triggered)
- * We use the **pc** to access the instruction memory
- * The **multiplexer** chooses between
 - * $pc + 4$
 - * `branchTarget`
- * It uses a control signal \rightarrow **isBranchTaken**

isBranchTaken


- * isBranchTaken is a **control** signal
 - * It is generated by the EX unit
- * Conditions on isBranchTaken

Instruction	Value of <i>isBranchTaken</i>
non-branch instruction	0
<i>call</i>	1
<i>ret</i>	1
<i>b</i>	1
<i>beq</i>	branch taken – 1 branch not taken – 0
<i>bgt</i>	branch taken – 1 branch not taken – 0

Data Path and Control Path

- * The **data path** consists of all the elements in a processor that are dedicated to storing, retrieving, and processing data such as **register files, memory, and the ALU**.
- * The **control path** primarily contains the **control unit**, whose role is to generate the appropriate signals to control the **movement of instructions**, and **data** in the data path.

Control Path

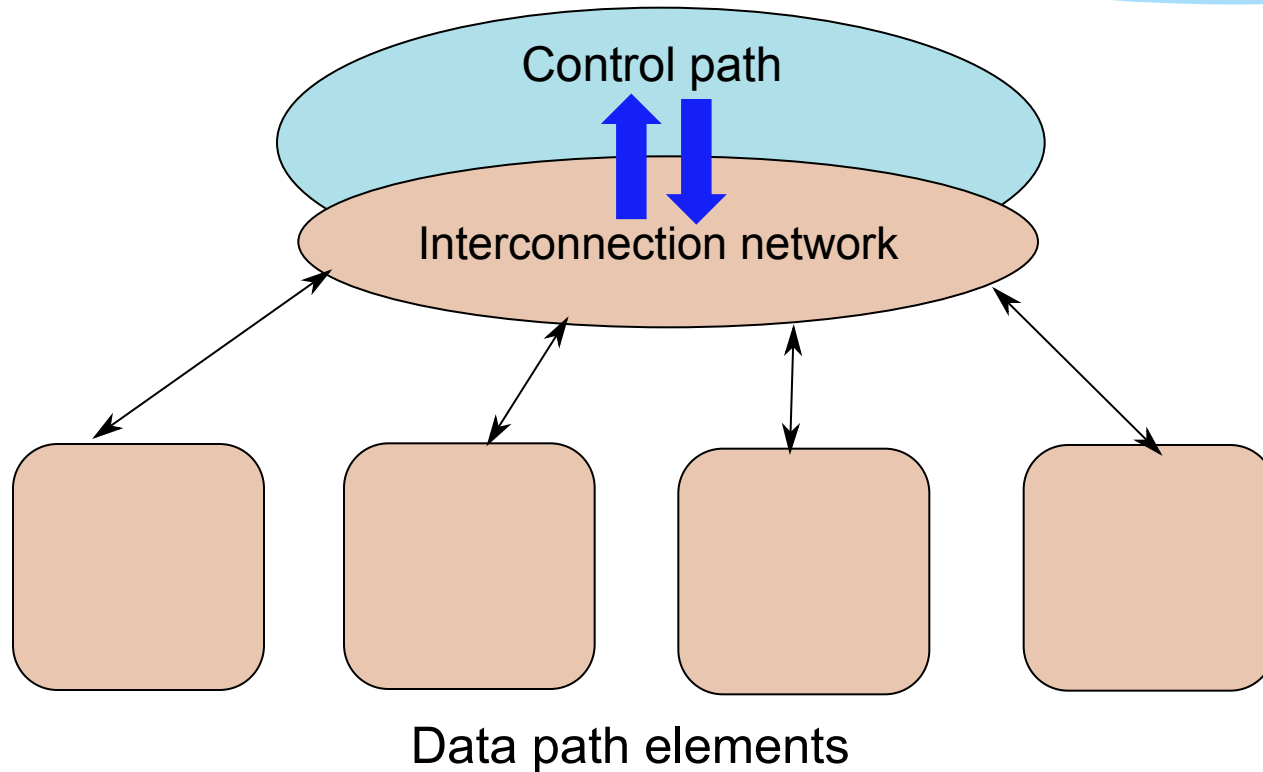

We will currently look at the hardwired control path.

Operand Fetch Unit


Inst.	Code	Format	Inst.	Code	Format
add	00000	add rd, rs1, (rs2/imm)	lsl	01010	lsl rd, rs1, (rs2/imm)
sub	00001	sub rd, rs1, (rs2/imm)	lsr	01011	lsr rd, rs1, (rs2/imm)
mul	00010	mul rd, rs1, (rs2/imm)	asr	01100	asr rd, rs1, (rs2/imm)
div	00011	div rd, rs1, (rs2/imm)	nop	01101	nop
mod	00100	mod rd, rs1, (rs2/imm)	ld	01110	ld rd, imm[rs1]
cmp	00101	cmprs1, (rs2/imm)	st	01111	st rd, imm[rs1]
and	00110	and rd, rs1, (rs2/imm)	beq	10000	beq offset
or	00111	or rd, rs1, (rs2/imm)	bgt	10001	bgt offset
not	01000	not rd, (rs2/imm)	b	10010	b offset
mov	01001	mov rd, (rs2/imm)	call	10011	call offset
			ret	10100	ret

Instruction Formats

Format	Definition					
<i>branch</i>	<i>op</i> (28-32)	<i>offset</i> (1-27)				
<i>register</i>	<i>op</i> (28-32)	<i>I</i> (27)	<i>rd</i> (23-26)	<i>rs1</i> (19-22)	<i>rs2</i> (15-18)	
<i>immediate</i>	<i>op</i> (28-32)	<i>I</i> (27)	<i>rd</i> (23-26)	<i>rs1</i> (19-22)	<i>imm</i> (1-18)	
<i>op</i> → opcode, <i>offset</i> → branch offset, <i>I</i> → immediate bit, <i>rd</i> → destination register						
<i>rs1</i> → source register 1, <i>rs2</i> → source register 2, <i>imm</i> → immediate operand						

- * Each format needs to be **handled** separately.

Register File Read

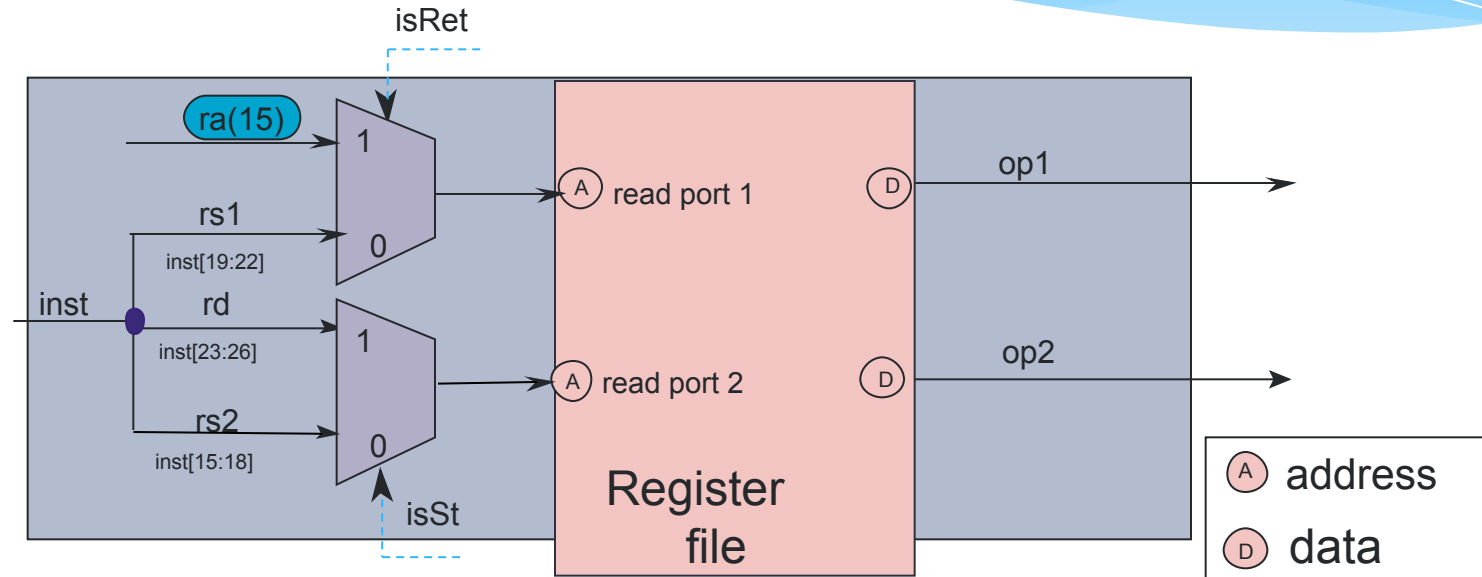


- * **First input** → *rs1* or *ra(15)* (ret instruction)
- * **Second input** → *rs2* or *rd* (store instruction)

Register File Access


- * The **register file** has two **read ports**
 - * 1st Input
 - * 2nd Input
- * The two outputs are op1, and op2
 - * **op1** is the **branch target (return address)** in the case of a **ret** instruction, or **rs1**
 - * **op2** is the value that needs to be stored in the case of a **store** instruction, or **rs2**

Immediate and Branch Unit

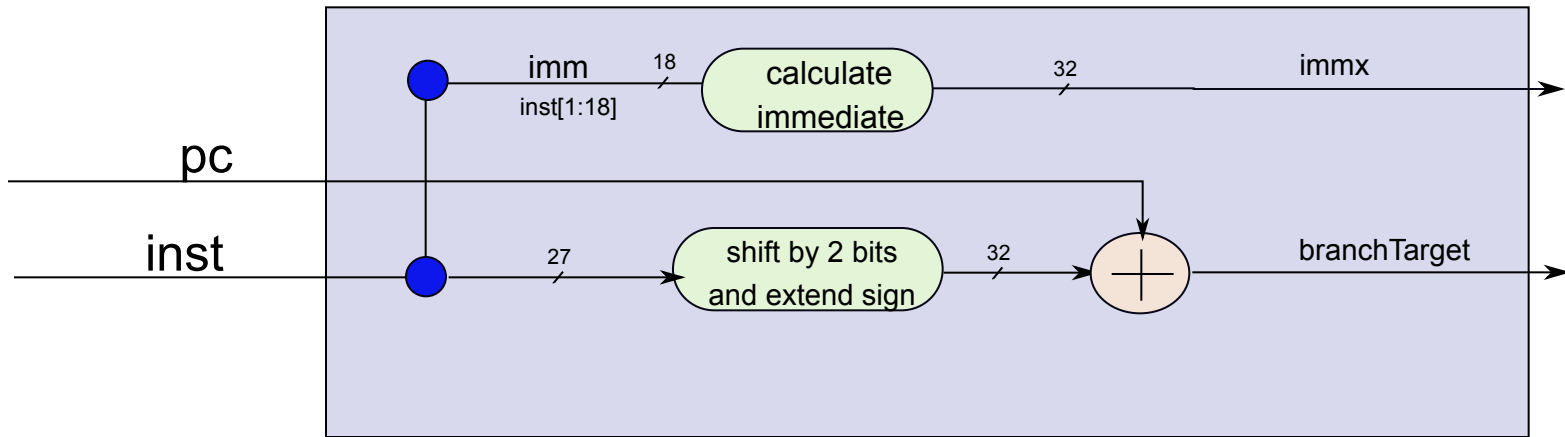


- * Compute **immx** (extended immediate), **branchTarget**, irrespective of the **instruction format**.
- * For the **branchTarget** we need to choose between the embedded target and op1 (ret)

OF Unit

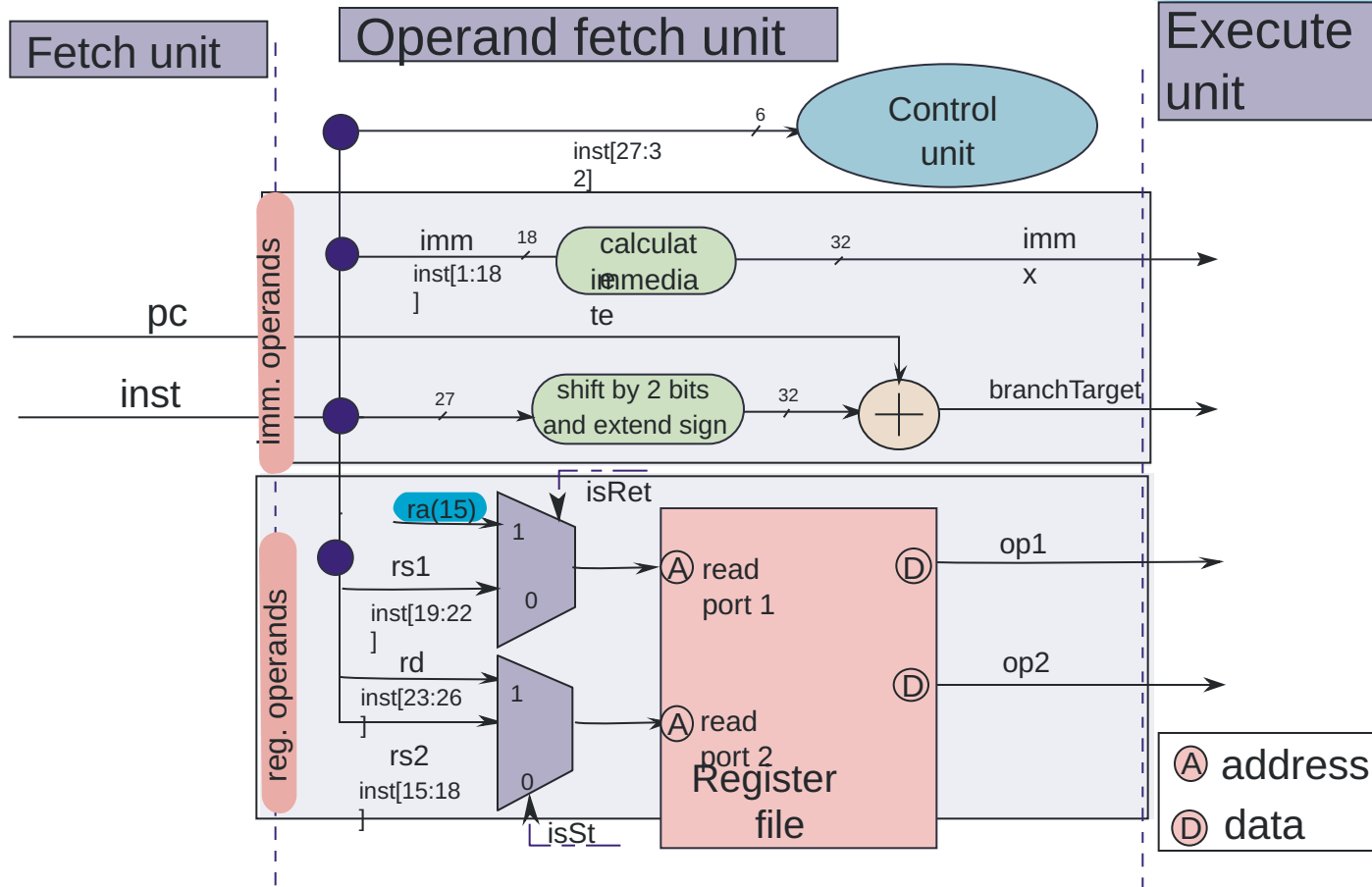


EX Stage – Branch Unit

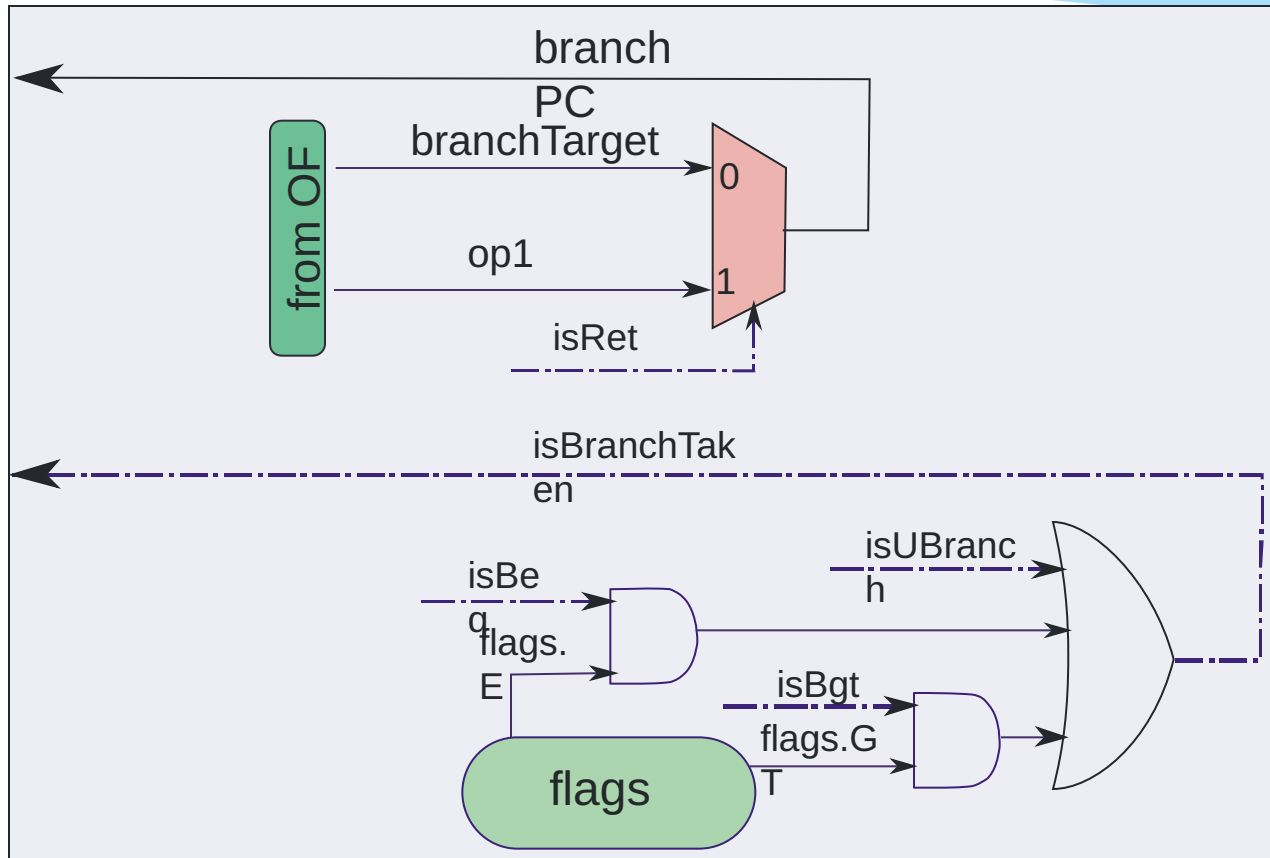


Generates the isBranchTaken Signal

ALU

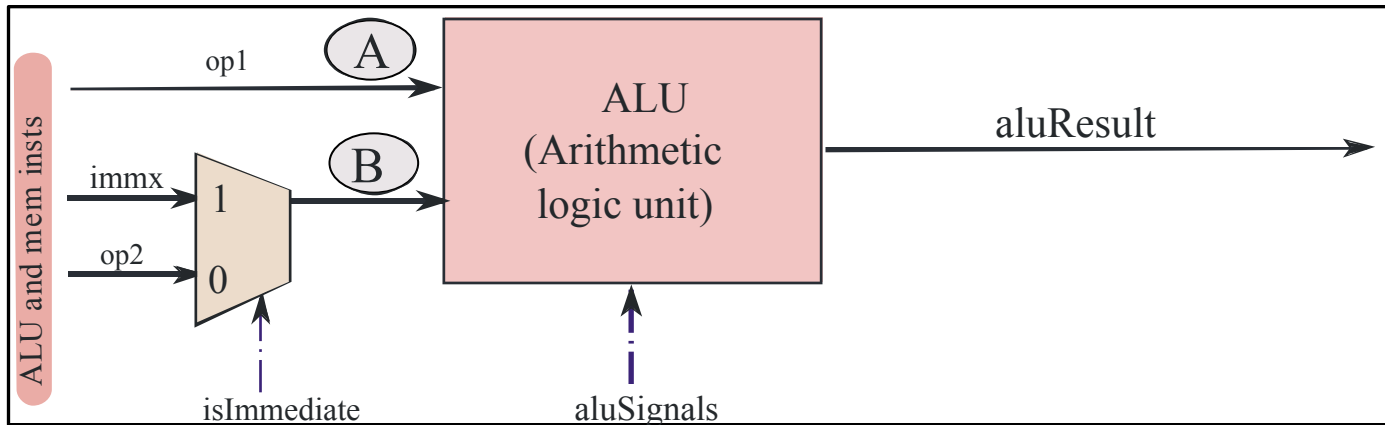

Choose between immx and op2 based on the value of the I bit


Inside the ALU

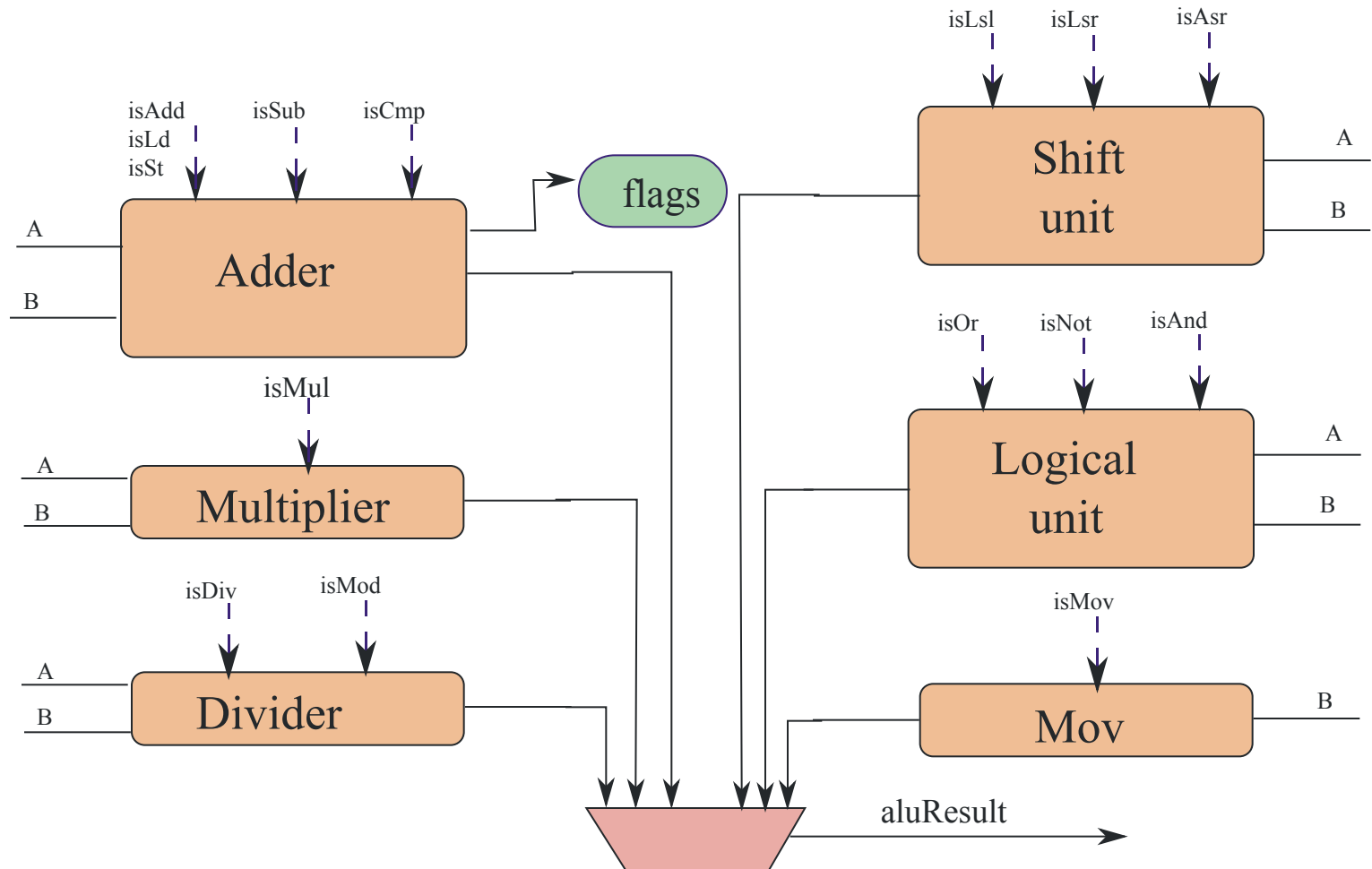

Disabling some Inputs


- * We do not want all the **units** of the ALU to be **active** at the same time because of we want to save **power**
- * The **instruction** will only use 1 **unit**
- * **Power** is dissipated when the **inputs** or **outputs** make a **transition** ($0 \rightarrow 1$, $1 \rightarrow 0$)
 - * We shall avoid a **transition** by not letting the new **inputs** to propagate to **units** that do not require them
 - * They will thus have the **old inputs** (**no** switching)

Use a Transmission Gate

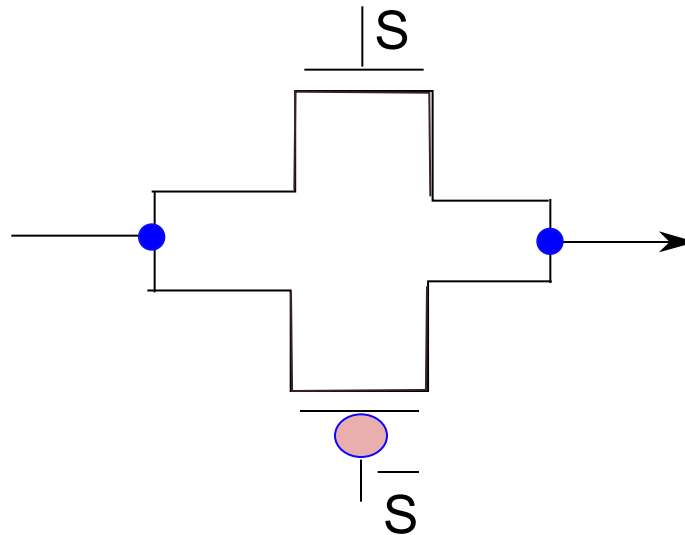


- * output = input (if $S = 1$)
- * Otherwise, the **output** is totally disconnected from the **input**


EX Unit

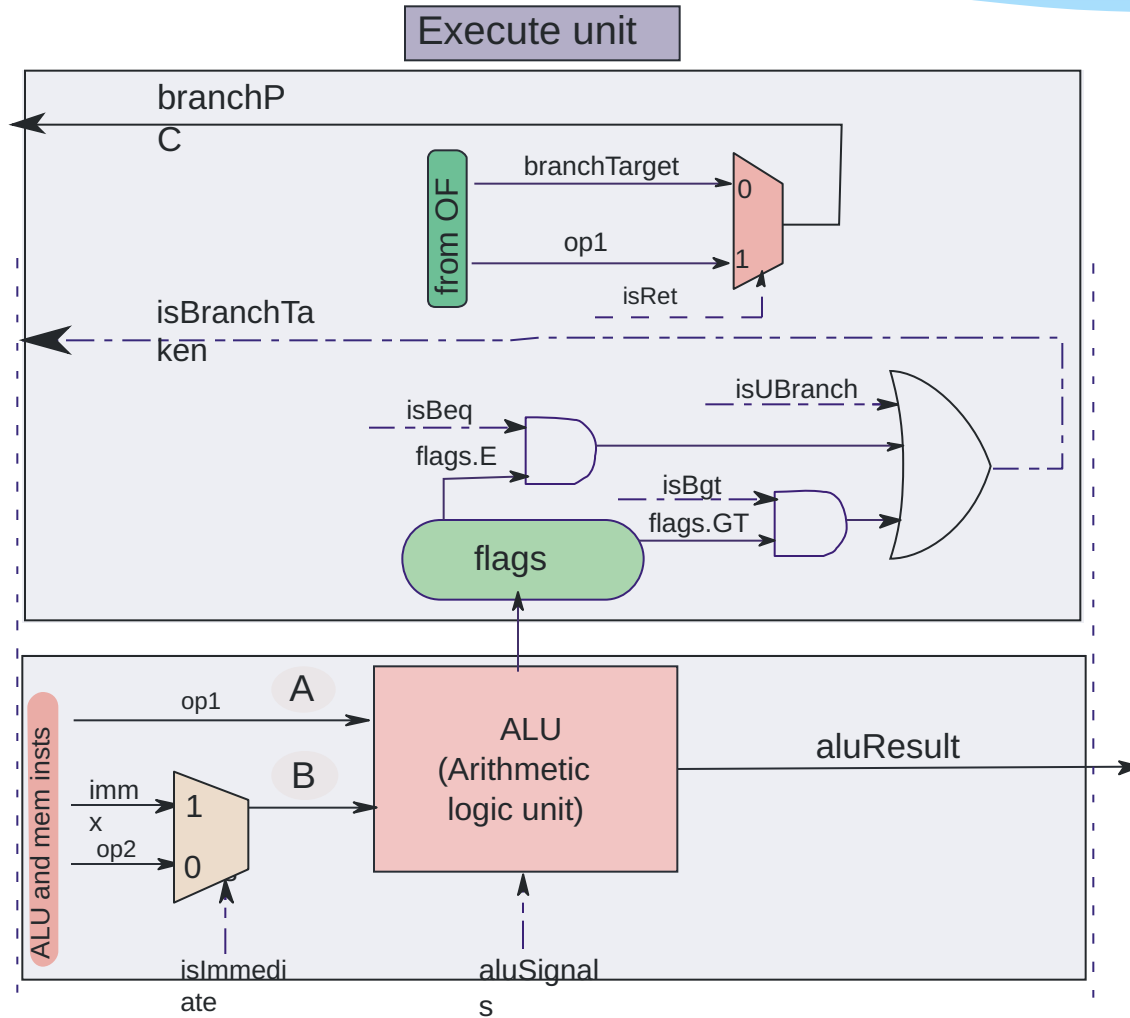


MA Unit

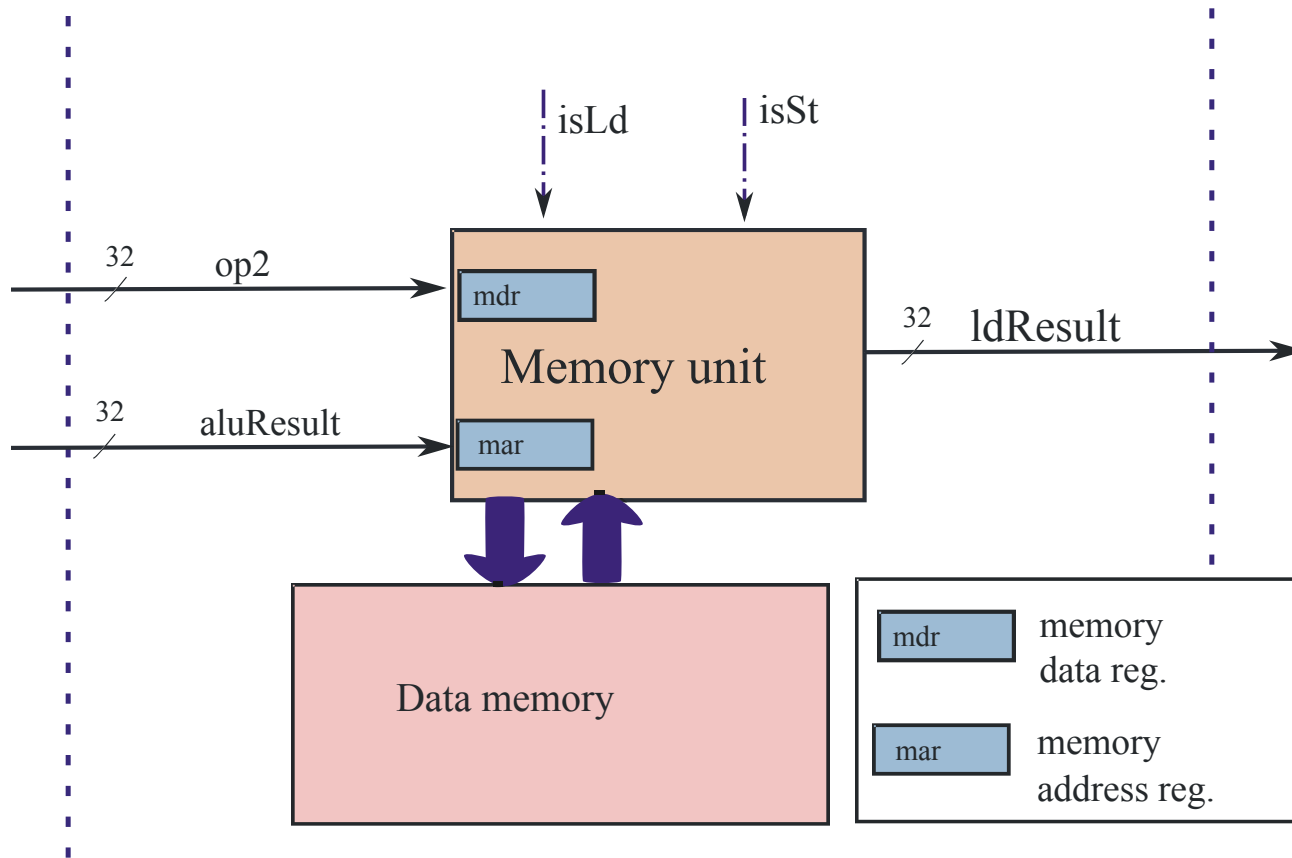


RW Unit

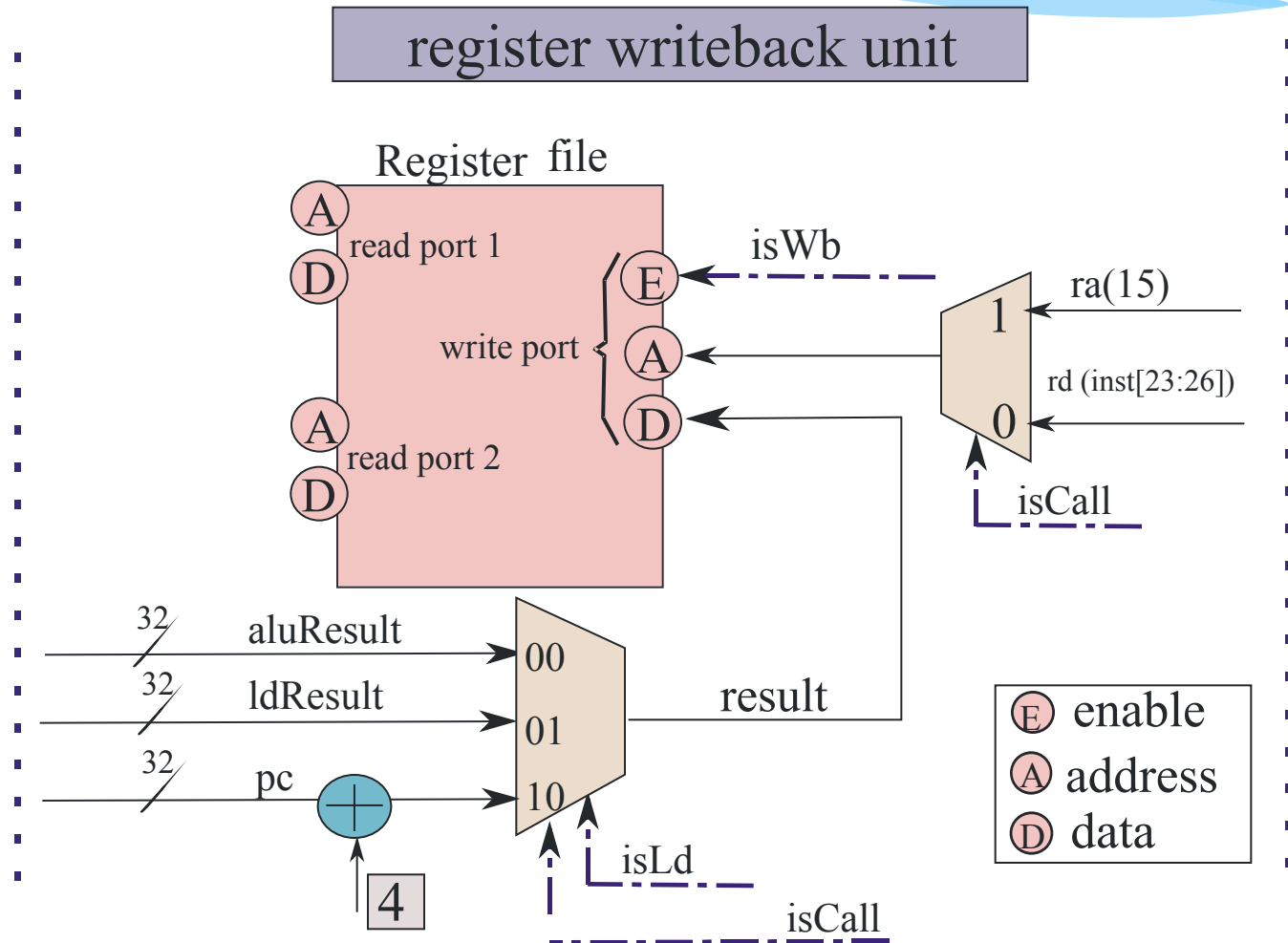

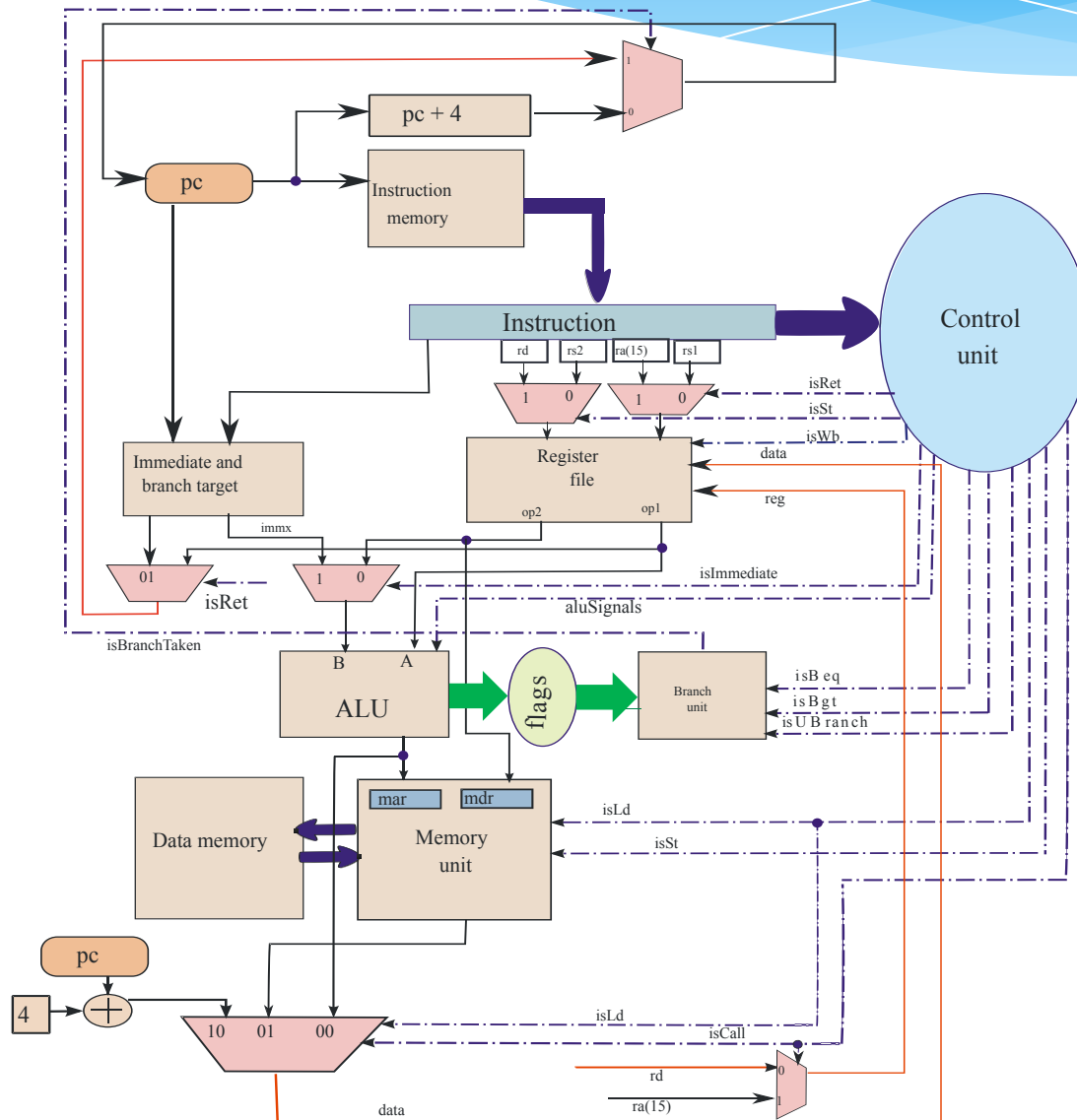


Outline

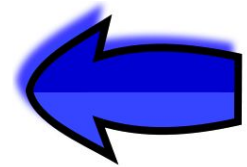- * Outline of a Processor
- * Detailed Design of each Stage
- * The Control Unit
- * Microprogrammed Processor
- * Microassembly Language
- * The Microcontrol Unit



The Hardwired Control Unit

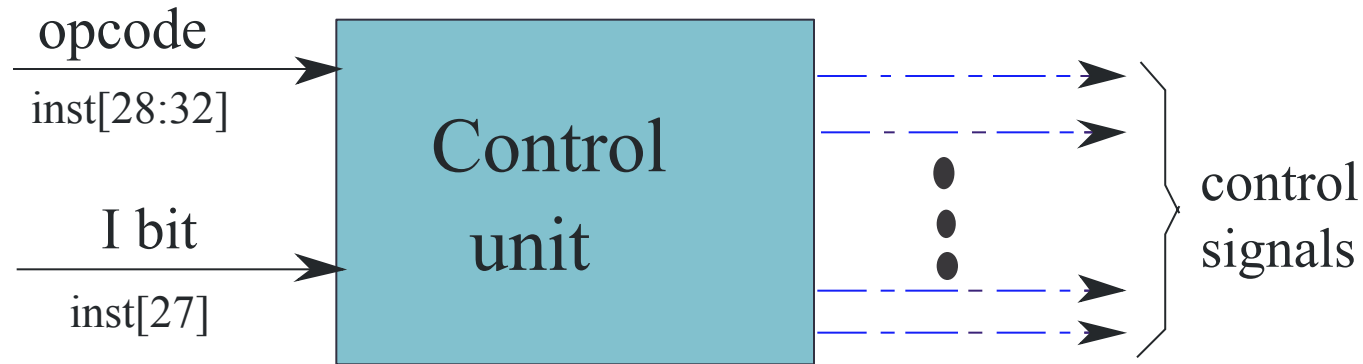

- * Given the **opcode** and the **immediate** bit
 - * It generates all the **control signals**


Control Signals

SerialNo.	Signal	Condition
1	<i>isSt</i>	Instruction: <i>st</i>
2	<i>isLd</i>	Instruction: <i>ld</i>
3	<i>isBeq</i>	Instruction: <i>beq</i>
4	<i>isBgt</i>	Instruction: <i>bgt</i>
5	<i>isRet</i>	Instruction:
6	<i>isImmediate</i>	rd bit set to 1
7	<i>isWb</i>	Instructions: <i>add, sub, mul, div, mod, and, or, not, mov, ld, lsl, lsr, asr, call</i>
8	<i>isUBranch</i>	Instructions: <i>b, call, ret</i>
9	<i>isCall</i>	Instructions: <i>call</i>

Control Signals – II

		<i>aluSignal</i>	
10	<i>isAdd</i>	Instructions: <i>add, ld, st</i>	
1	<i>isSub</i>	Instruction: <i>sub</i>	
12	<i>isCmp</i>	Instruction: <i>cmp</i>	
13	<i>isMul</i>	Instruction: <i>mul</i>	
14	<i>isDiv</i>	Instruction: <i>div</i>	
15	<i>isMod</i>	Instruction: <i>mod</i>	
16	<i>isLsl</i>	Instruction: <i>lsl</i>	
17	<i>isLsr</i>	Instruction: <i>lsr</i>	
18	<i>isAsr</i>	Instruction: <i>asr</i>	
19	<i>isOr</i>	Instruction:	
20	<i>isAnd</i>	Instruction:	
21	<i>isNot</i>	Instruction: <i>not</i>	
22	<i>isMov</i>	Instruction: <i>mov</i>	

Control signal Logic

 

Serial No.	Signal	Condition
1	<i>isSt</i>	$\overline{op_5} \cdot op_4 \cdot op_3 \cdot op_2 \cdot op_1$
2	<i>isLd</i>	$\overline{op_5} \cdot op_4 \cdot op_3 \cdot op_2 \cdot \overline{op_1}$
3	<i>isBeq</i>	$op_5 \cdot \overline{op_4} \cdot \overline{op_3} \cdot \overline{op_2} \cdot \overline{op_1}$
4	<i>isBgt</i>	$op_5 \cdot op_4 \cdot op_3 \cdot op_2 \cdot op_1$
5	<i>isRet</i>	$op_5 \cdot \overline{op_4} \cdot op_3 \cdot \overline{op_2} \cdot \overline{op_1}$
6	<i>isImmediate</i>	<i>I</i>
7	<i>isWb</i>	$\sim(op_5 + \overline{op_5} \cdot op_3 \cdot op_1 \cdot (op_4 + \overline{op_2})) + op_5 \cdot \overline{op_4} \cdot \overline{op_3} \cdot op_2 \cdot op_1$
8	<i>isUbranch</i>	$op_5 \cdot \overline{op_4} \cdot (\overline{op_3} \cdot op_2 + op_3 \cdot \overline{op_2} \cdot \overline{op_1})$
9	<i>isCall</i>	$op_5 \cdot op_4 \cdot op_3 \cdot op_2 \cdot op_1$

Control Signal Logic - II

<i>aluSignals</i>		
10	<i>isAdd</i>	$\overline{op5}.\overline{op4}.\overline{op3}.\overline{op2}.\overline{op1} + \overline{op5}.op4.op3.op2$
11	<i>isSub</i>	$\overline{op5}.\overline{op4}.\overline{op3}.\overline{op2}.op1$
12	<i>isCmp</i>	$\overline{op5}.\overline{op4}.op3.\overline{op2}.op1$
13	<i>isMul</i>	$\overline{op5}.\overline{op4}.\overline{op3}.op2.\overline{op1}$
14	<i>isDiv</i>	$\overline{op5}.\overline{op4}.\overline{op3}.op2.op1$
15	<i>isMod</i>	$\overline{op5}.\overline{op4}.op3.\overline{op2}.\overline{op1}$
16	<i>isLsl</i>	$\overline{op5}.op4.\overline{op3}.op2.\overline{op1}$
17	<i>isLsr</i>	$\overline{op5}.op4.op3.\overline{op2}.\overline{op1}$
18	<i>isAsr</i>	$\overline{op5}.op4.op3.op2.\overline{op1}$
19	<i>isOr</i>	$\overline{op5}.\overline{op4}.op3.op2.\overline{op1}$
20	<i>isAnd</i>	$\overline{op5}.op4.\overline{op3}.\overline{op2}.\overline{op1}$
21	<i>isNot</i>	$\overline{op5}.op4.op3.\overline{op2}.op1$
22	<i>isMov</i>	$\overline{op5}.op4.op3.op2.op1$

Processor State

Memory	
Address	Contents
...	
...	
0x00000010	0x00004880
0x00000014	0x00020caf
...	


Flags Reg	Eq=0; GT=0
------------------	------------

Register File	
Name	Contents
r0	0x00000010
r1	0x00000020
r2	0x00000030
r3	0x00000100
...	

PC	0x00000010
-----------	------------

Outline

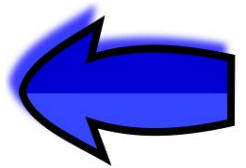- * Outline of a Processor
- * Detailed Design of each Stage
- * The Control Unit
- * Microprogrammed Processor
- * Microassembly Language
- * The Microcontrol Unit




Microprogramming

- * Idea of **microprogramming**
 - * Expose the elements in a processor to software
 - * Implement instructions as dedicated software routines
- * Why make the **implementation** of instructions flexible ?
 - * Dynamically **change** their behaviour
 - * Fix bugs in **implementations**
 - * Implement very **complex** instructions

Microprogrammed Data Path


- * Expose all the state elements to dedicated system software – **firmware**
- * Write dedicated routines in **firmware** for implementing each instruction
- * **Basic idea**
 - * 1 SimpleRisc Instruction → Several micro instructions
 - * Execute each micro instruction
 - * We require a microprogram counter, and microinstruction memory

Fetch Unit

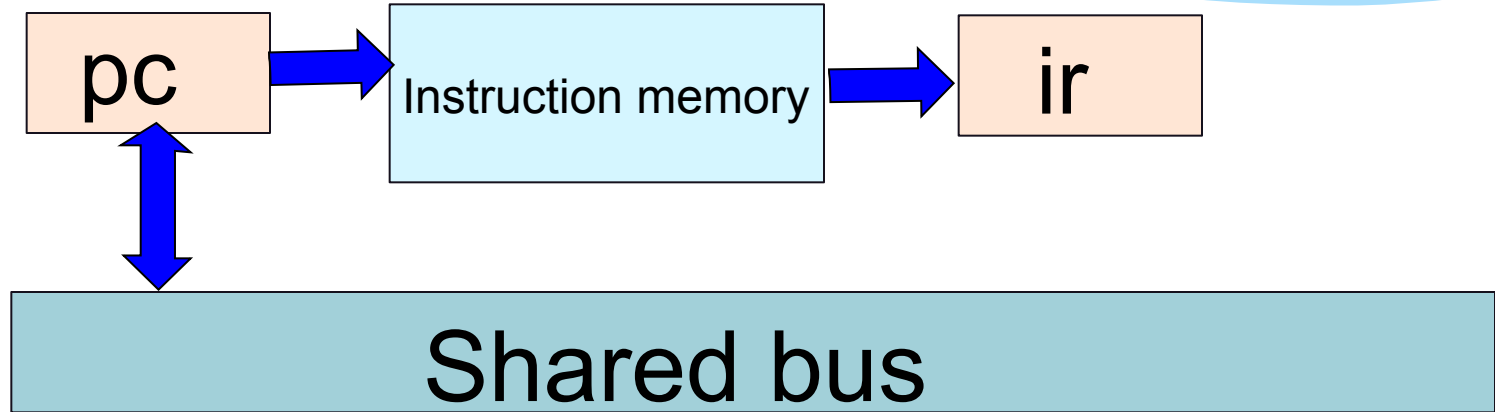


- * The **pc** is used to access the instruction memory.
- * The contents of the instruction are saved in the **instruction register (ir)**

Decode Unit

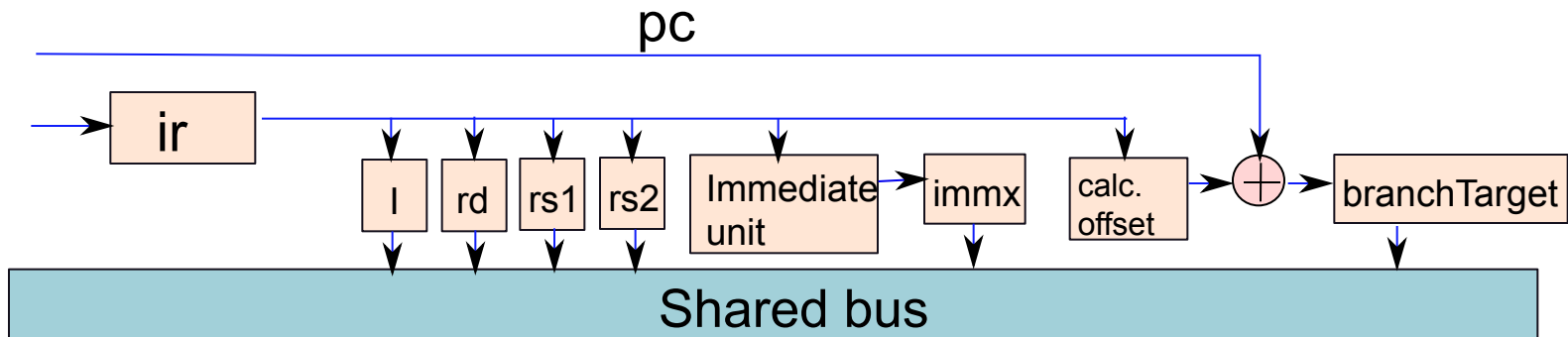


- * Divide the contents of **ir** into different fields
 - * I, rd, rs1, rs2, immx, and branchTarget

The Register File

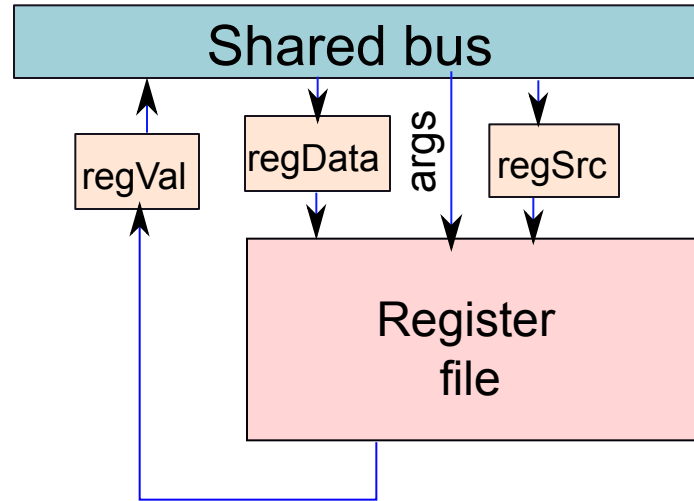


- * **regSrc** (id of the source/dest register)
- * **regData** (data to be stored)
- * **regVal** (register value)

ALU

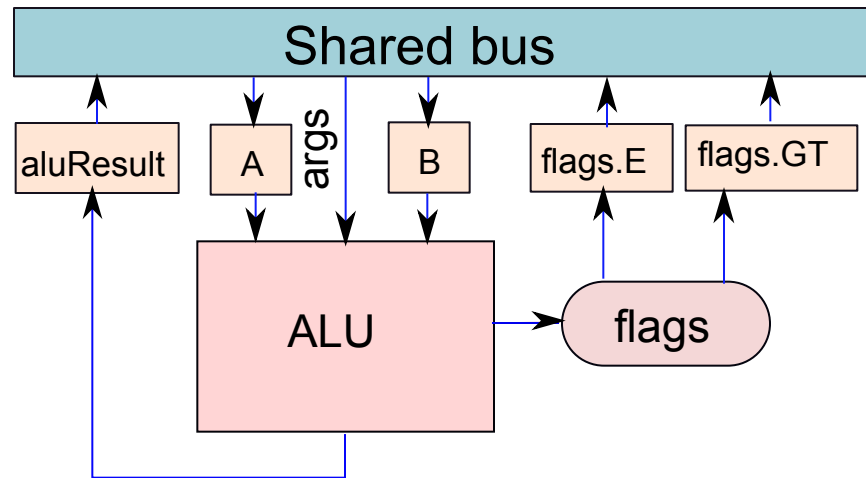


- * A, B \rightarrow ALU operands
- * args \rightarrow ALU operation type
- * aluResult \rightarrow ALU Result

Memory Unit

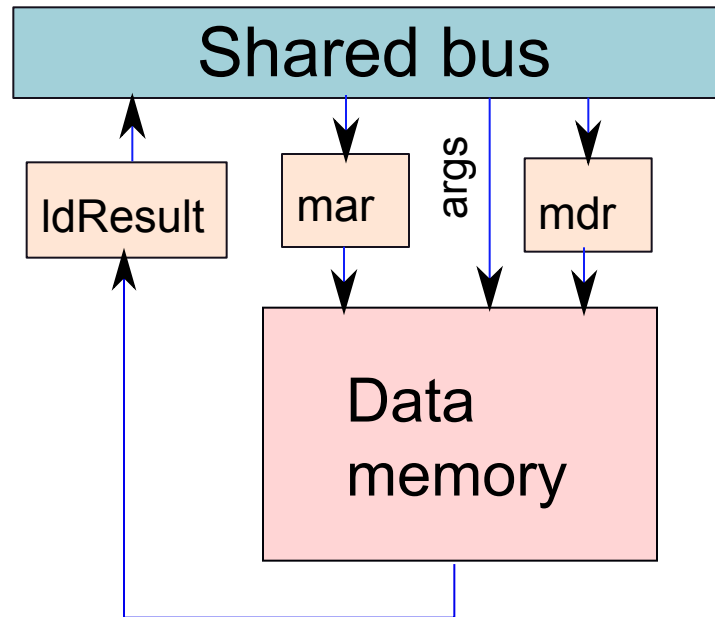


Microprogrammed Data Path

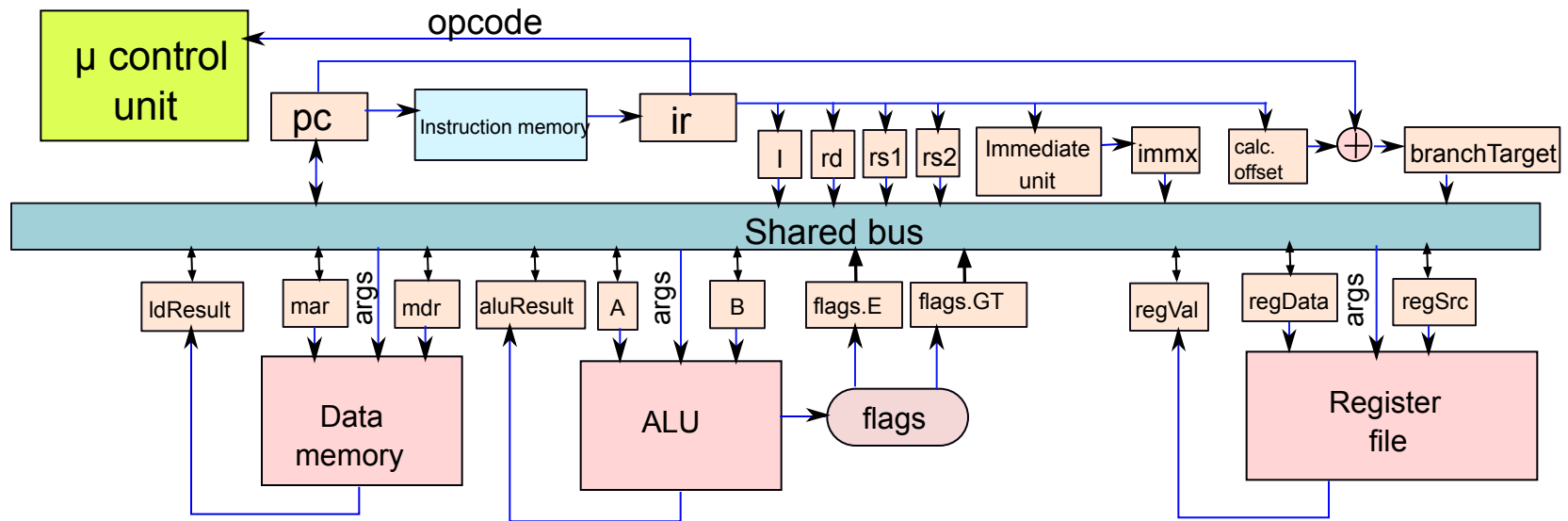

Outline

 - * Outline of a Processor
- * Detailed Design of each Stage
- * The Control Unit
- * Microprogrammed Processor
- * Microassembly Language
- * The Microcontrol Unit



Internal Registers

SerialNo.	Register	Size (bits)	Function
1	<i>pc</i>	32	program counter
2	<i>ir</i>	32	instruction register
3	<i>I</i>	1	immediate bit in the instruction
4	<i>r</i>	4	destination register id
5	<i>rs 1</i>	4	id of the first source register
6	<i>rs 2</i>	4	id of the second source register
7	<i>immx</i>	32	immediate embedded in the instruction (after processing modifiers)
8	<i>branchTarget</i>	32	branch target, computed as the sum of the PC and the offset embedded in the instruction
9	<i>regSrc c</i>	4	contains the id of the register that needs to be accessed in the register file
10	<i>regData</i>	32	contains the data to be written into the register file

Internal Registers - II

11	<i>regVal</i>	32	value read from the register file
12	<i>A</i>	32	first operand of the ALU
13	<i>B</i>	32	second operand of the ALU
14	<i>flags.E</i>	1	the equality flag
15	<i>flags.GT</i>	1	the greater than flag
16	<i>aluResult</i>	32	the ALU result
17	<i>mar</i>	32	memory address register
18	<i>mdr</i>	32	memory data register
19	<i>ldResult</i>	32	the value loaded from memory

Microinstructions

Basic Instructions

- * **mloadIR** → Loads the instruction register (ir) with the contents of the instruction.
- * **mdecode** → Waits for 1 cycle. Meanwhile, all the decode registers get populated
- * **mswitch** → Loads the set of micro instructions corresponding to a program instruction.

Move Microinstructions

- * **mmov** r1, r2 : $r1 \leftarrow r2$
- * **mmov** r1, r2, <args> : $r1 \leftarrow r2$, send the value of **args** on the bus
- * **mmovi** r1, <imm> : $r1 \leftarrow \text{imm}$

Add and Branch Microinstructions

- * **madd** r1, imm, <args>

- * $r1 \leftarrow r1 + \text{imm}$

- * send <args> on the bus

- * **mbeq** r1, imm, <label>

- * if ($r1 == \text{imm}$), $\mu\text{pc} = \text{addr}(\text{label})$

- * **mb** <label>

- * $\mu\text{pc} = \text{addr}(\text{label})$

Summary of Microinstructions

SerialNo.	Microinstruction	Semantics
1	<i>mloadIR</i>	$ir \leftarrow [pc]$
2	<i>mdecode</i>	populate all the decode registers
3	<i>mswitch</i>	jump to the μpc corresponding to the opcode
4	<i>mmov reg1, reg2, < args ></i>	$reg1 \leftarrow reg2$, send the value of <i>args</i> to the unit that owns <i>reg1</i> , <i>< args ></i> is optional
5	<i>mmovi reg1, imm, < args ></i>	$reg1 \leftarrow imm$, <i>< args ></i> is optional
6	<i>madd reg1, imm, < args ></i>	$reg1 \leftarrow reg1 + imm$, <i>< args ></i> is optional
7	<i>mbeq reg1, imm, < label ></i>	if ($reg1 = imm$) $\mu pc \leftarrow addr(label)$
8	<i>mb <label></i>	$\mu pc \leftarrow addr(label)$

Implementing Instructions in Microcode

* The microcode preamble

```
.begin:  
mloadIR  
mdecode  
madd pc, 4  
mswitch
```

- * Load the program counter
- * Decode the instruction
- * Add 4 to the pc
- * Switch to the first microinstruction in the microcode sequence of the prog. instruction

3 Address Format ALU Instruction

```
/* transfer the first operand to the ALU */
mmov regSrc, rs1, <read>
mmov A, regVal

/* check the value of the immediate register */
mbeq I, 1, .imm
/* second operand is a register */
mmov regSrc, rs2, <read>
mmov B, regVal, <aluop>
mb .rw
/* second operand is an immediate */
.imm:
mmov B, immx, <aluop>

/* write the ALU result to the register file*/
.rw:
mmov regSrc, rd
mmov regData, aluResult, <write>
mb .begin
```


The mov Instruction

—mov instruction—

```
/* check the value of the immediate register */
mbeq I, 1, .imm
/* second operand is a register */
mmov regSrc, rs2, <read>
mmov regData, regVal
mb .rw
/* second operand is an immediate */
.imm:
mmov regData, immx

/* write to the register file*/
.rw:
mmov regSrc, rd, <write>

/* jump to the beginning */
mb .begin
```

The not Instruction

— not instruction —

```
/* check the value of the immediate register */
mbeq I, 1, .imm
/* second operand is a register */
mmov regSrc, rs2, <read>
mmov B, regVal, <not> /* ALU operation */
mb .rw
/* second operand is an immediate */
.imm:
mmov B, immx, <not> /* ALU operation */

/* write to the register file*/
.rw:
mmov regData, aluResult
mmov regSrc, rd, <write>

/* jump to the beginning */
mb .begin
```

The *cmp* Instruction

— *cmp* instruction —

```
/* transfer rs1 to register A */  
mov regSrc, rs1, <read>  
mov A, regVal  
  
/* check the value of the immediate register  
mbeq I, 1, .imm  
  
/* second operand is a register */  
mmov regSrc, rs2, <read>  
mmov B, regVal, <cmp> /* ALU operation */  
mb .begin  
  
/* second operand is an immediate */  
.imm:  
mmov B, immx, <cmp> /* ALU operation */  
mb .begin
```

The *nop* Instruction

- * `mb .begin`

The *ld* Instruction

—— *ld* instruction ——

```
/* transfer rs1 to register A */  
mmov regSrc, rs1, <read>  
mmov A, regVal  
  
/* calculate the effective address */  
mmov B, immx, <add> /* ALU operation */  
  
/* perform the load */  
mmov mar, aluResult, <load>  
  
/* write the loaded value to the register file */  
mmov regData, ldResult  
mmov regSrc, rd, <write>  
  
/* jump to the beginning */  
mb .begin
```

The *st* Instruction

— *st* instruction —

```
/* transfer rs1 to register A */  
mmov regSrc, rs1, <read>  
mmov A, regVal  
  
/* calculate the effective address */  
mmov B, immx, <add> /* ALU operation */  
  
/* perform the store */  
mmov mar, aluResult  
mmov regSrc, rd, <read>  
mmov mdr, regVal, <store>  
  
/* jump to the beginning */  
mb .begin
```

beq and *bgt* Instructions

—*beq* instruction—

```
/* test the flags register  
mbeq flags.E, 1, .branch  
mb .begin
```

```
.branch:  
mmov pc, branchTarget  
mb .begin
```

—*bgt* instruction—

```
/* test the flags register  
mbeq flags.GT, 1, .branch  
mb .begin
```

```
.branch:  
mmov pc, branchTarget  
mb .begin
```

call Instruction

call instruction

```
/* save PC + 4 in the return address register */  
mmov regData, pc  
mmovi regSrc, 15, <write>  
  
/* branch to the function */  
mmov pc, branchTarget  
mb .begin
```


ret Instruction

ret instruction

```
/* save the contents of the return  
   address register in the PC */
```

```
mmovi regSrc, 15, <read>  
mmov pc, regVal  
mb .begin
```

Example

Change the call instruction to store the return address on the stack. The preamble need not be shown.

Answer:

```

      stack based call instruction
/* read the stack pointer */
mmovi regSrc, 14, <read>
madd regVal, -4 /* decrement the stack pointer */

/* set the memory address to the stack pointer */
mmov mar, regVal


/* update the stack pointer */
mmov regData, regVal, <write> /* update stack pointer */

/* write the return address to the stack */
mmov mdr, pc, <store>


/* jump to the beginning */
mb .begin
```

Outline

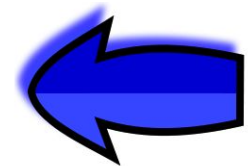- * Outline of a Processor
- * Detailed Design of each Stage
- * The Control Unit
- * Microprogrammed Processor
- * Microassembly Language
- * The Microcontrol Unit



Shared Bus

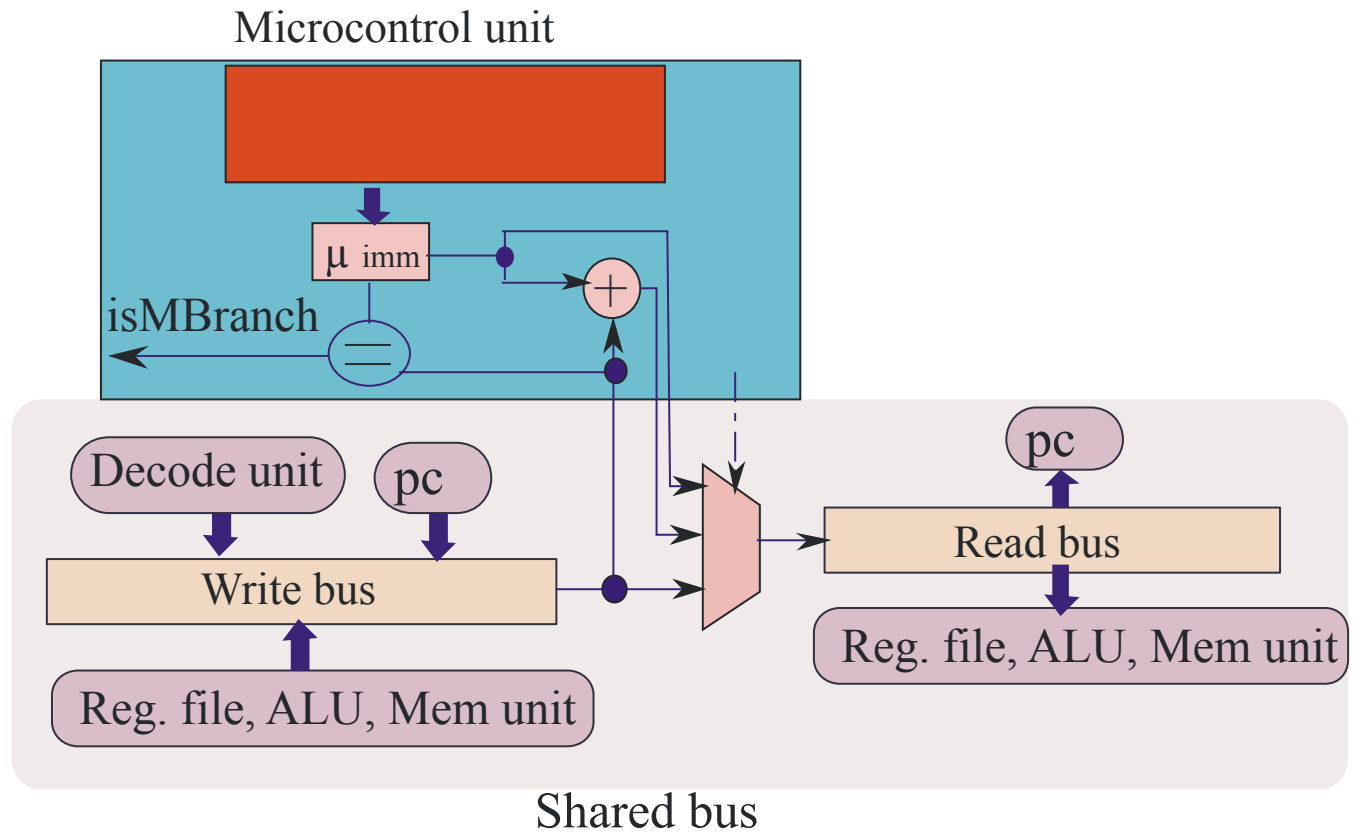

Encoding an Instruction

- * **Vertical Microprogramming** (45 bit inst.)
 - * 3 bits → type of instruction
 - * 5 bits → source register
 - * 5 bits → destination register
 - * 12 bits → immediate
 - * 10 bit → branch target in microcode memory
 - * 10 bit → args value
 - * 3 bits → (unit id)
 - * 7 bits → operation code


Horizontal Microprogramming

- * Encoding


- * 10 bits → branch target
- * 12 bits → immediate
- * 10 bits → args
- * 33 bits → bit vector of all the control signals

- * Total size of the encoded instruction : 65 bits

Vertical Microprogramming

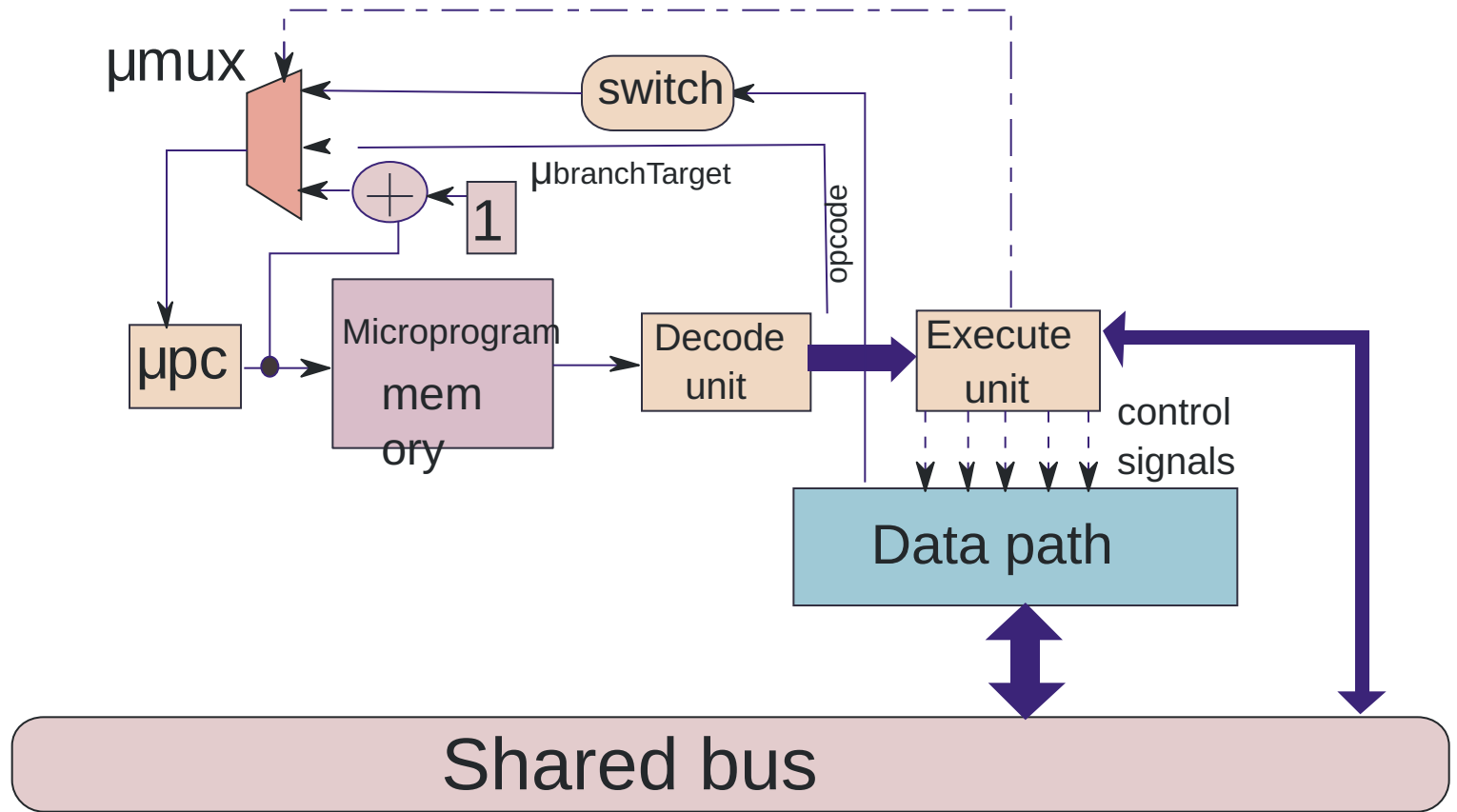

Horizontal Microprogramming

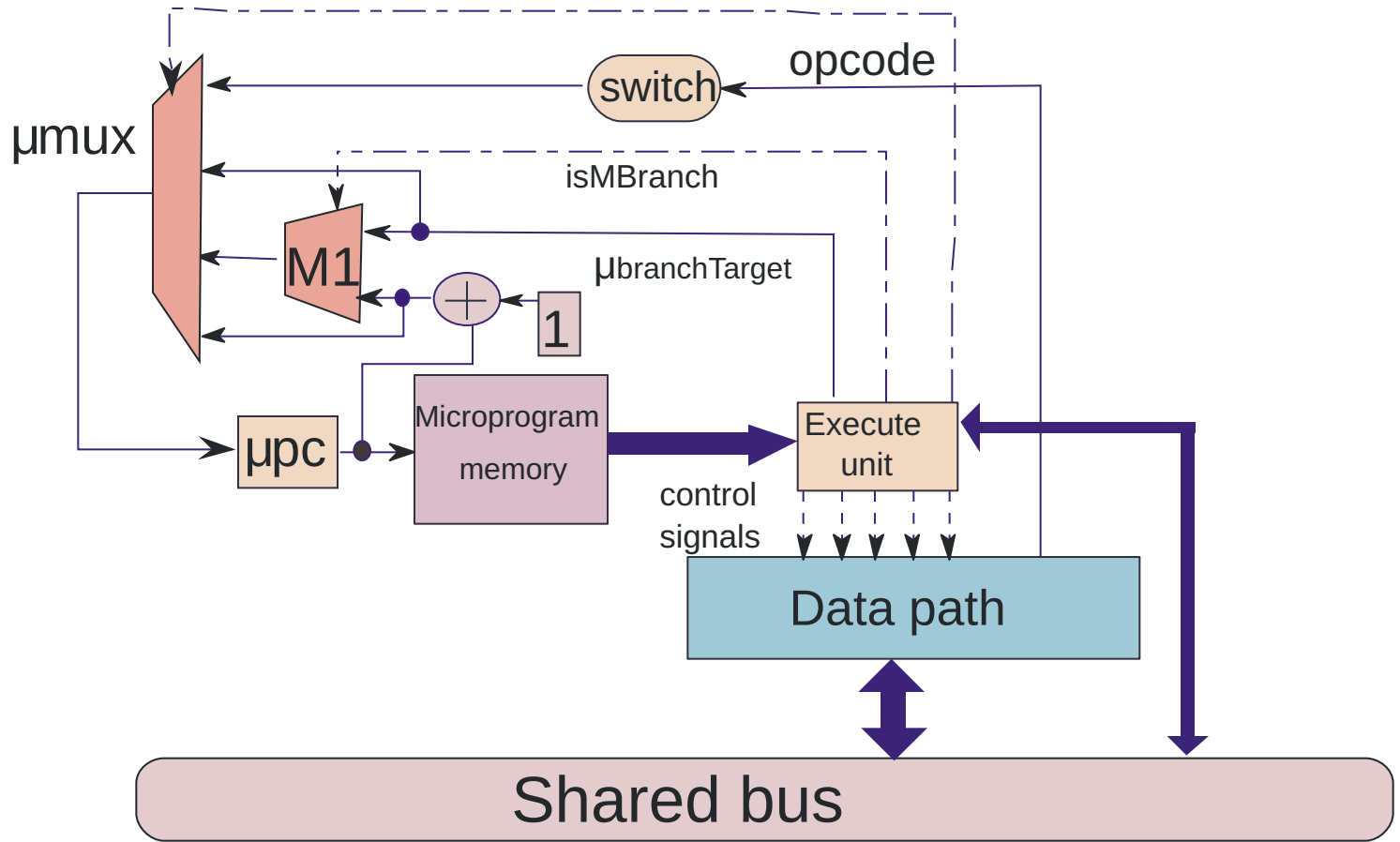



THE END